

HW IV

Design a serial adder. It takes 8-bit inputs A and B and adds them in a serial fashion when the **go(start)** input is set to 1. The result of the operation is stored in a 9-bit sum register.

A block diagram of the circuit is shown in **Figure** below. It consists of three shift registers, a full-adder, a flip-flop to store carry-out signal from the full adder and a finite state machine (FSM). The shift registers A and B are loaded with the values of A and B . After the **start** signal is set high, these registers are shifted right one bit at a time. At the same time the least-significant bits of A and B are added and the result is stored into the shift register sum . Once all bits of A and B have been added, the circuit stops and displays the sum until a new addition is requested.

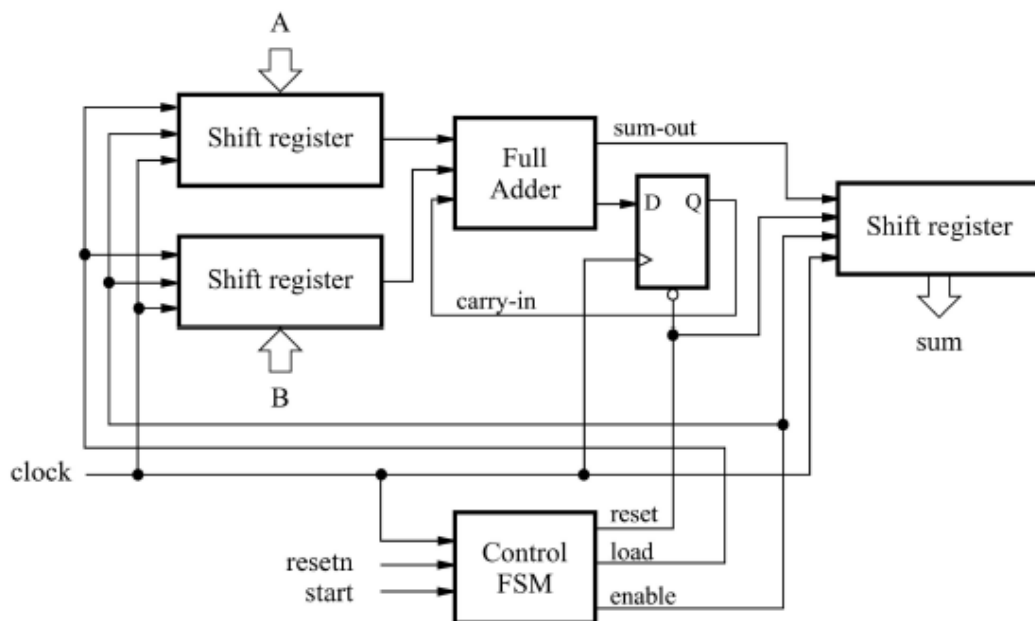


Figure. Block diagram of a serial adder circuit